



A magnitude comparator is a combinational circuit that compares two numbers A and B and determines whether one number is greater than, less than, or equal to the other number.

1-bit magnitude comparator

Let us assume that the two input variables are A & B. The output of the comparison is specified by three binary variables that are whether $A > B$ or $A = B$ or $A < B$. The truth table of a 1-bit magnitude comparator is as follow

A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0


The output functions can be derived from the truth table

$$A > B = A\bar{B}$$

$$(A = B) = \bar{A}\bar{B} + AB$$

$$A < B = \bar{A}B$$

 These functions are implemented by basic logic gates



2-bit Magnitude Comparator

Following the same procedure, we can design a 2-bit magnitude comparator. The truth table of this circuit is shown below:

A ₁	A ₀	B ₁	B ₀	A > B	A = B	A < B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

The k-maps of the three outputs are

		$B_1 B_0$			
		00	01	11	10
$A_1 A_0$	00				
	01	1			
	11	1	1		1
	10	1	1		

A > B

		$B_1 B_0$			
		00	01	11	10
$A_1 A_0$	00	1			
	01		1		
	11			1	
	10				1

A = B

		$B_1 B_0$			
		00	01	11	10
$A_1 A_0$	00		1	1	1
	01			1	1
	11				
	10			1	

A < B

The three functions can be derived from k-map

$$A > B = A_0 \overline{B_1} \overline{B_0} + A_1 \overline{B_1} + A_1 A_0 \overline{B_0}$$

$$A = B = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 A_0 B_1 B_0 + A_1 \overline{A_0} B_1 \overline{B_0}$$


$$= \overline{A_1} \overline{B_1} (\overline{A_0} \overline{B_0} + A_0 B_0) + A_1 B_1 (A_0 B_0 + \overline{A_0} \overline{B_0})$$

$$= (A_0 B_0 + \overline{A_0} \overline{B_0}) (A_1 B_1 + \overline{A_1} \overline{B_1})$$

$$= (A_0 \oplus B_0)' (A_1 \oplus B_1)'$$

$$A < B = \overline{A_1} B_1 + \overline{A_0} B_1 B_0 + \overline{A_1} \overline{A_0} B_0$$

 This can be implemented by the following logic gates



Multi-Bit Comparator

As the number of bits increases, it is obvious that the design process becomes more complex. However, multi-bit comparator can be designed by using 1-bit comparator with a set of logic gates.

Consider two numbers, A and B , with four digits each.


$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

The two numbers are equal if all pairs of significant digits are equal. That is $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$, $A_0 = B_0$

To determine whether A is greater or less than B , we inspect the relative pairs starting from the most significant position (MSB).

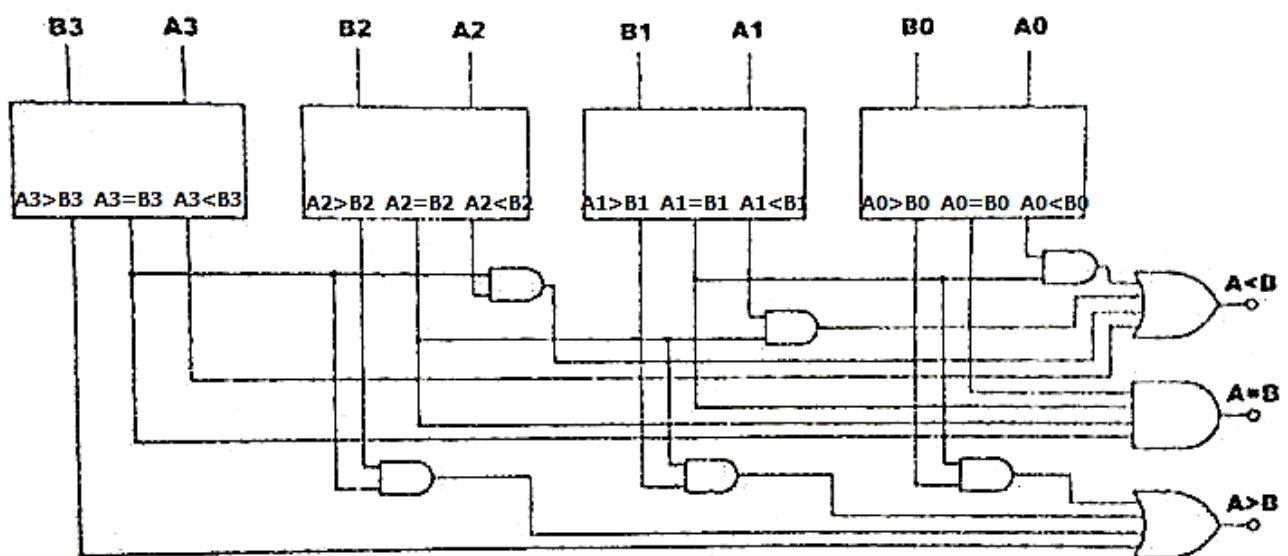If the two MSBs are equal, we compare the next lower significant pair of digits. The comparison continues until we reach the last bit in the number (LSB).



Code Conversion – Part II

BCD to 2421 code

2421 code is a self-complementary code, that is, the 9's complement of the decimal number is obtained by changing the 1s to 0s and 0s to 1s. The 2421 code is the same as that in BCD from 0 to 4. However, it varies from 5 to 9.

The Truth Table is as follow

Decimal Equivalent	Input variables				Output variables			
	BCD code				2421 code			
	W	X	Y	Z	A	B	C	D
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	0
3	0	0	1	1	0	0	1	1
4	0	1	0	0	0	1	0	0
5	0	1	0	1	1	0	1	1
6	0	1	1	0	1	1	0	0
7	0	1	1	1	1	1	0	1
8	1	0	0	0	1	1	1	0
9	1	0	0	1	1	1	1	1

The K-Map of the 4-output variables can be obtained from the truth table

	Y'Z'	Y'Z	YZ	YZ'
W'X'				
W'X		1	1	1
WX	X	X	X	X
WX'	1	1	X	X

Karnaugh map for A.

	Y'Z'	Y'Z	YZ	YZ'
W'X'				
W'X	1		1	1
WX	X	X	X	X
WX'	1	1	X	X

Karnaugh map for B.

	Y'Z'	Y'Z	YZ	YZ'
W'X'			1	1
W'X		1		
WX	X	X	X	X
WX'	1	1	X	X

Karnaugh map for C.

	Y'Z'	Y'Z	YZ	YZ'
W'X'		1	1	
W'X		1	1	
WX		X	X	
WX'		1	X	

Karnaugh map for D.

$$A = W + XZ + XY$$

$$B = W + X\bar{Z} + XY$$

$$C = W + X\bar{Y}Z + \bar{X}Y$$

$$D = Z$$

The logic diagram can be implemented using basic logic gates **(H.W)**