



## Multiplexer


A multiplexer is a combinational circuit that selects one inputs from many input lines and directs it to a **single output** line. It also has another input called **Selector (S)**.

Normally, there are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.
 
### 2-1 multiplexer


A 2-1 multiplexer has two data input lines, one output line and one selection line  $S$ .

- When  $S = 0$ , the upper input  $I_0$  will be transferred to the output.
- When  $S = 1$ , the lower input  $I_1$  will be transferred to the output.



### Truth Table

Selection Input	Input		Output
S	I <sub>0</sub>	I <sub>1</sub>	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

 

$$Y = \bar{S}I_0 + SI_1$$

### 4-1 multiplexer


A 4-1 multiplexer has 4 data input lines, one output line and two selection line  $S_1, S_0$ .

Selection Inputs		Input Channels				Output
$S_1$	$S_0$	$I_0$	$I_1$	$I_2$	$I_3$	Y
0	0	0	X	X	X	0
0	0	1	X	X	X	1
0	1	X	0	X	X	0
0	1	X	1	X	X	1
1	0	X	X	0	X	0
1	0	X	X	1	X	1
1	1	X	X	X	0	0
1	1	X	X	X	1	1

$S_1$	$S_0$	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

$$Y = \overline{S_1} \overline{S_0} I_0 + \overline{S_1} S_0 I_1 + S_1 \overline{S_0} I_2 + S_1 S_0 I_3$$


### Logic Diagram

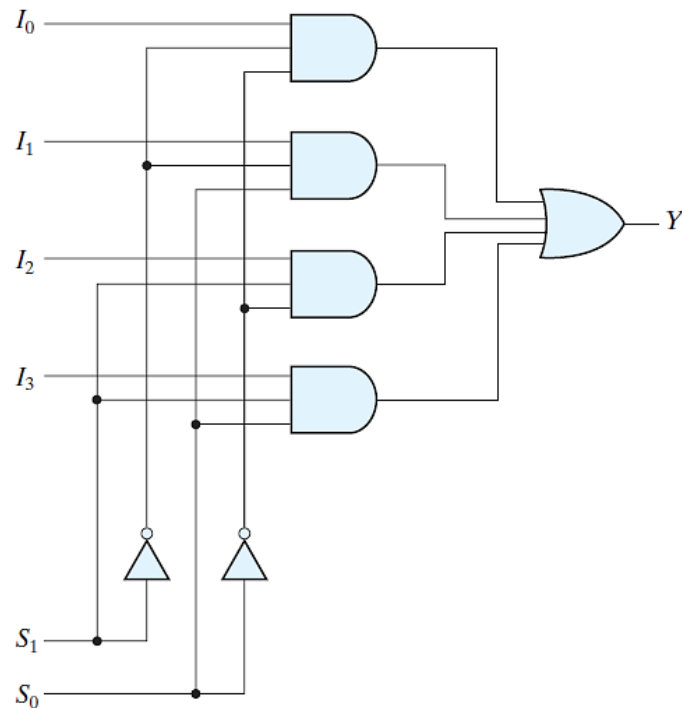

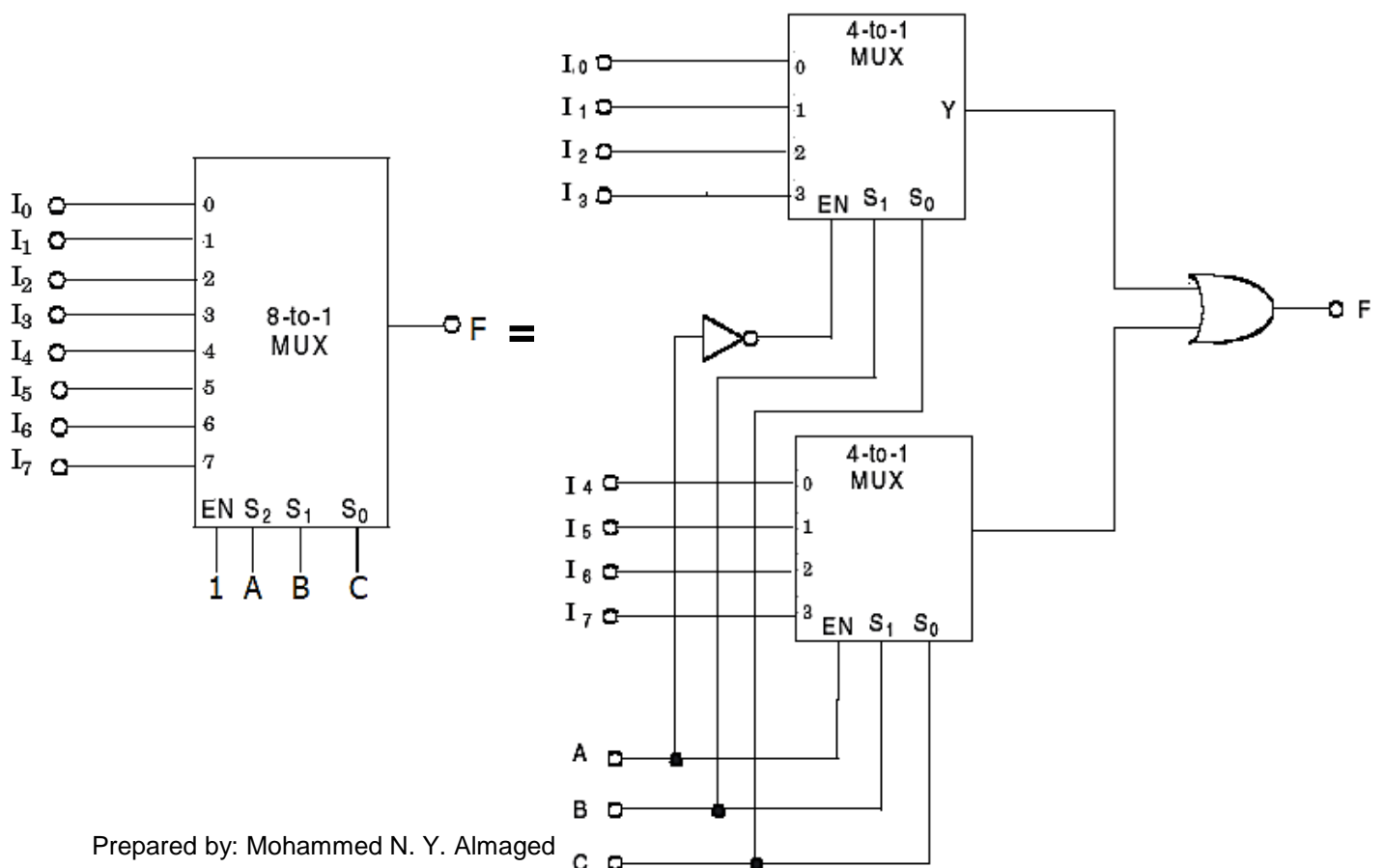
### Cascading of Multiplexers

Multiplexers of a larger number of inputs can be implemented by the multiplexers of a smaller number of input lines.

Ex) Design an 8-1 multiplexer by using two 4-1 multiplexers.



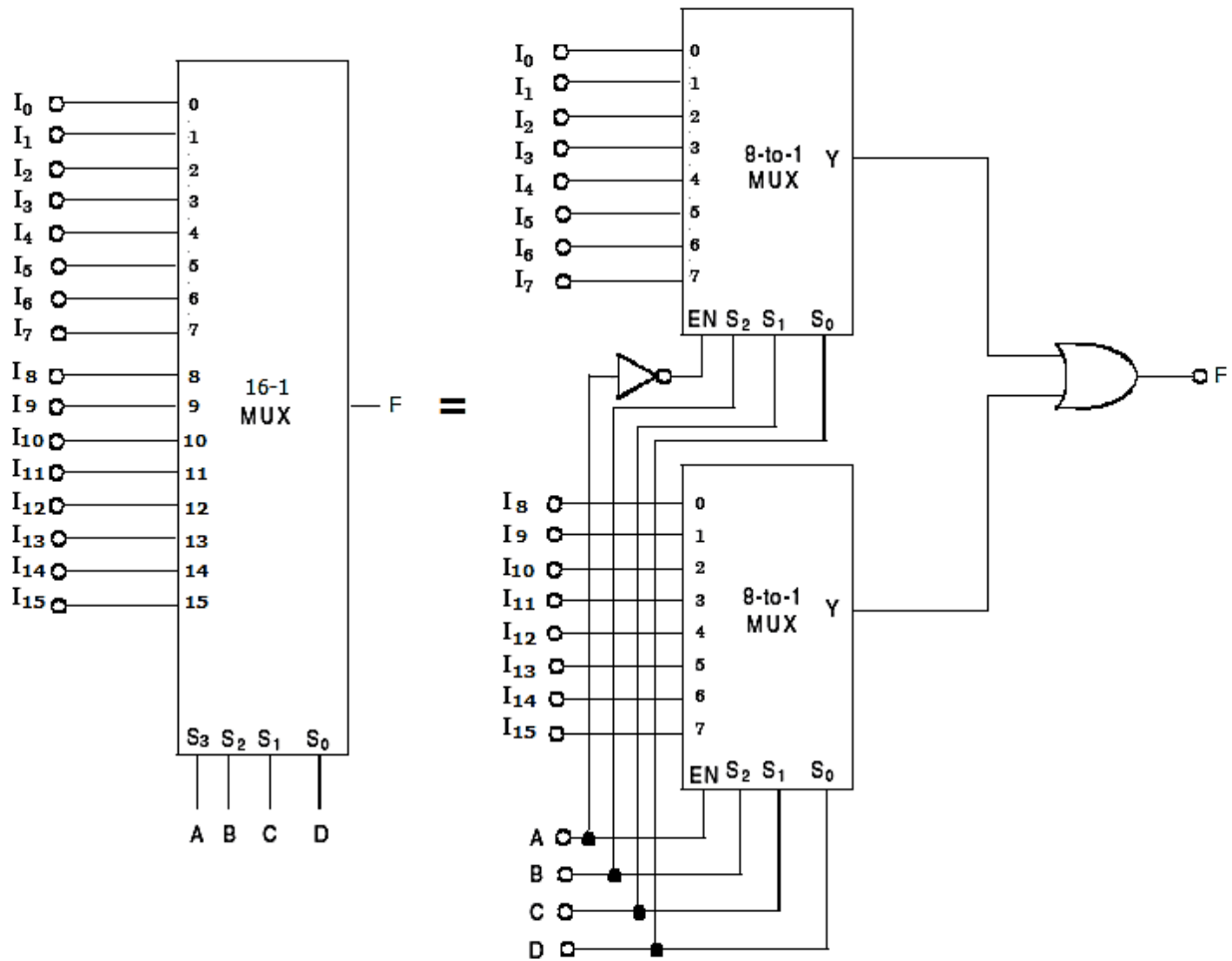Ex) Design a 16-1 multiplexer by using two 8-1 multiplexers.



HW) Design a 16-1 multiplexer by using 2-1 multiplexers.

### Boolean Function Implementation

A Boolean function of  $n$  variables, for example  $(x, y, z)$ , can be implemented with a multiplexer that has  $n - 1$  selection inputs ( $S_1$  &  $S_0$ ). The first  $n - 1$  variables of the function  $(x, y)$  are connected to the selection inputs of the multiplexer ( $S_1$  &  $S_0$ ). The remaining single variable ( $z$ ) of the function is used for the data inputs ( $I_0, I_1, I_2, I_3$ ).

The relationship between the remaining variable ( $z$ ) and the data inputs of the multiplexer ( $I$ ) is determined from the **truth table**. Each data input of the multiplexer will be either equal to  $Z, \bar{Z}, 0, 1$

Ex) Design the  $F(x, y, z) = \sum(1, 2, 6, 7)$  using Multiplexer.

This function of three variables can be implemented with a multiplexer that has 2 selectors, thus we use 4 -1 multiplexer.

X is connected to  $S_1$


Y is connected to  $S_0$

Then, we find the relationship between  $Z$  and the data inputs  $I_0, I_1, I_2, I_3$  from the truth table as follow:

**Truth Table**

$x$	$y$	$z$	$F$	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

**Logic Diagram**

 

**Ex)** Design the  $F(A, B, C, Z) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$  using Multiplexer.

This function of 4 variables can be implemented with a multiplexer that has 3 selectors, thus we use 8 -1 multiplexer.

A is connected to  $S_2$ , B is connected to  $S_1$ , C is connected to  $S_0$

Then, we find the relationship between D and the data inputs  $I_0 - I_7$  from the truth table as follow:

**Truth Table**

**Logic Diagram**

$A$	$B$	$C$	$D$	$F$	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

