



جامعة نينوى
كلية هندسة الإلكترونيات

Circuit Design with VHDL 10

Textbook: Volnei A. Pedroni

Submitted By: Hussein Aideen


VHDL> Examples

- Signed and Unsigned Comparators

```
1  ---- Signed Comparator: -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE ieee.std_logic_arith.all;  -- necessary!
5  -----
6  ENTITY comparator IS
7      GENERIC (n: INTEGER := 7);
8      PORT (a, b: IN SIGNED (n DOWNT0 0);
9            x1, x2, x3: OUT STD_LOGIC);
10 END comparator;
11 -----
12 ARCHITECTURE signed OF comparator IS
13 BEGIN
14     x1 <= '1' WHEN a > b ELSE '0';
15     x2 <= '1' WHEN a = b ELSE '0';
16     x3 <= '1' WHEN a < b ELSE '0';
17 END signed;
18 -----
```

VHDL> Examples

 - Parallel-to-Serial Converter
- circuit operation:
 - when $\text{load} = 1$ the data must stored in the register.
 - when $\text{load} = 0$ the registerd data shifted out to dout each time clk goes from 0 to 1.



VHDL> Examples

- Parallel-to-Serial Converter

```
1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY serial_converter IS
6      PORT ( d: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
7            clk, load: IN STD_LOGIC;
8            dout: OUT STD_LOGIC);
9  END serial_converter;
10 -----
```


VHDL> Examples

- Parallel-to-Serial Converter

```
11 ARCHITECTURE serial_converter OF serial_converter IS
12     SIGNAL reg: STD_LOGIC_VECTOR (7 DOWNT0 0);
13 BEGIN
14     PROCESS (clk)
15     BEGIN
16         IF (clk'EVENT AND clk='1') THEN
17             IF (load='1') THEN reg <= d;
18             ELSE reg <= reg(6 DOWNT0 0) & '0';
19             END IF;
20         END IF;
21     END PROCESS;
22     dout <= reg(7);
23 END serial_converter;
24 -----
```


VHDL> Examples

- Signal Generators

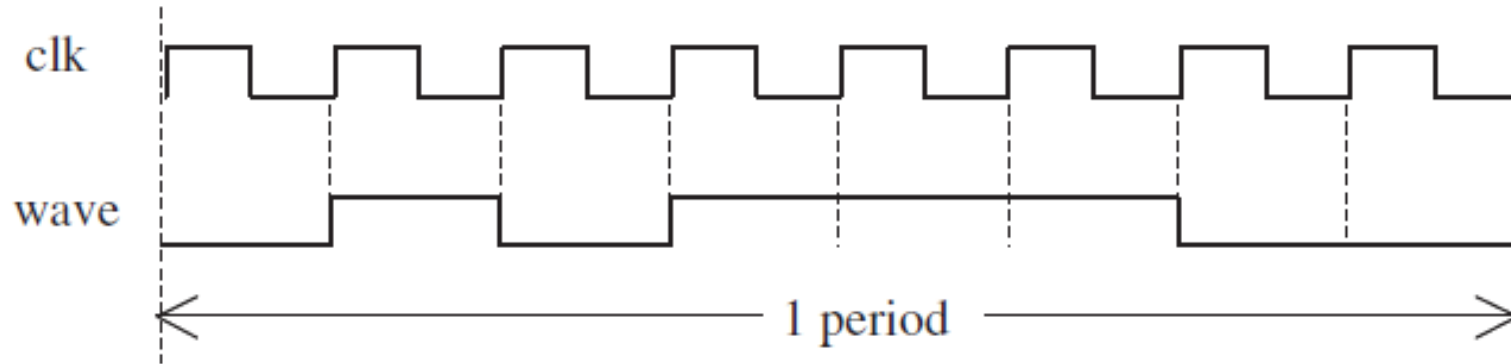

VHDL> Examples

- Signal Generators

 

```
1  -----  
2  LIBRARY ieee;  
3  USE ieee.std_logic_1164.all;  
4  -----  
5  ENTITY signal_gen1 IS  
6      PORT (clk: IN BIT;  
7            wave: OUT BIT);  
8  END signal_gen1;  
9  -----
```

VHDL> Examples

- Signal Generators

```
10 ARCHITECTURE arch1 OF signal_gen1 IS
11 BEGIN
12     PROCESS
13         VARIABLE count: INTEGER RANGE 0 TO 7;
14     BEGIN
15         WAIT UNTIL (clk'EVENT AND clk='1');
16         CASE count IS
17             WHEN 0 => wave <= '0';
18             WHEN 1 => wave <= '1';
19             WHEN 2 => wave <= '0';
20             WHEN 3 => wave <= '1';
21             WHEN 4 => wave <= '1';
22             WHEN 5 => wave <= '1';
23             WHEN 6 => wave <= '0';
24             WHEN 7 => wave <= '0';
25         END CASE;
26         count := count + 1;
27     END PROCESS;
28 END arch1;
29 -----
```