



جامعة نينوى
كلية هندسة الإلكترونيات

Circuit Design with VHDL 11

Textbook: Volnei A. Pedroni


Submitted By: Hussein Aideen

VHDL> State Machines


- Finite state machines (FSM) constitute a special modeling technique for sequential logic circuits.
- helpful in the design of certain types of systems, (digital controllers, counters, for example).

VHDL> State Machines

 - Mealy machine: the output of the machine depends not only on the present state but also on the current input.



 - Moore machine: the output depends only on the current state.



VHDL> State Machines

 


Figure 8.1
Mealy (Moore) state machine diagram.

VHDL> State Machines

Design Style #1:

- the design of the lower section is completely separated from that of the upper section.

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----
ENTITY <entity_name> IS
    PORT ( input: IN <data_type>;
          reset, clock: IN STD_LOGIC;
          output: OUT <data_type>);
END <entity_name>;
-----
ARCHITECTURE <arch_name> OF <entity_name> IS
    TYPE state IS (state0, state1, state2, state3, ...);
    SIGNAL pr_state, nx_state: state;
BEGIN
```

VHDL> State Machines

Design of the Lower (Sequential) Section:

```
PROCESS (reset, clock)
BEGIN
    IF (reset='1') THEN
        pr_state <= state0;
    ELSIF (clock'EVENT AND clock='1') THEN
        pr_state <= nx_state;
    END IF;
END PROCESS;
```

VHDL> State Machines

Design of the Upper (Combinational) Section:

```
PROCESS (input, pr_state)
BEGIN
    CASE pr_state IS
        WHEN state0 =>
            IF (input = ...) THEN
                output <= <value>;
                nx_state <= state1;
            ELSE ...
            END IF;
        WHEN state1 =>
            IF (input = ...) THEN
                output <= <value>;
                nx_state <= state2;
            ELSE ...
            END IF;
        WHEN state2 =>
            IF (input = ...) THEN
                output <= <value>;
                nx_state <= state3;
            ELSE ...
            END IF;
        ...
    END CASE;
END PROCESS;
END <arch_name>;
```

VHDL> State Machines

Example

Example 8.2: Simple FSM #1

Figure 8.4 shows the states diagram of a very simple FSM. The system has two states (stateA and stateB), and must change from one to the other every time $d = '1'$ is received. The desired output is $x = a$ when the machine is in stateA, or $x = b$ when in stateB. The initial (reset) state is stateA.

 


Figure 8.4
State machine of example 8.1.

VHDL> State Machines

```
1  -----
2  ENTITY simple_fsm IS
3      PORT ( a, b, d, clk, rst: IN BIT;
4              x: OUT BIT);
5  END simple_fsm;
6  -----
7  ARCHITECTURE simple_fsm OF simple_fsm IS
8      TYPE state IS (stateA, stateB);
9      SIGNAL pr_state, nx_state: state;
10 BEGIN
11     ----- Lower section: -----
12     PROCESS (rst, clk)
13     BEGIN
14         IF (rst='1') THEN
15             pr_state <= stateA;
16         ELSIF (clk'EVENT AND clk='1') THEN
17             pr_state <= nx_state;
18         END IF;
19     END PROCESS;
```

VHDL> State Machines

```
20  ----- Upper section: -----
21  PROCESS (a, b, d, pr_state)
22  BEGIN
23      CASE pr_state IS
24          WHEN stateA =>
25              x <= a;
26              IF (d='1') THEN nx_state <= stateB;
27              ELSE nx_state <= stateA;
28              END IF;
29          WHEN stateB =>
30              x <= b;
31              IF (d='1') THEN nx_state <= stateA;
32              ELSE nx_state <= stateB;
33              END IF;
34      END CASE;
35  END PROCESS;
36 END simple_fsm;
```

VHDL> State Machines

Design Style #2 (Stored Output):

- In #1: Notice that in this case, if it is a Mealy machine (one whose output is dependent on the current input), the output might change when the input changes (asynchronous output).
- To make Mealy machines synchronous.

VHDL> State Machines

Design Style #2 (Stored Output):

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----
ENTITY <ent_name> IS
    PORT (input: IN <data_type>;
          reset, clock: IN STD_LOGIC;
          output: OUT <data_type>);
END <ent_name>;

-----
ARCHITECTURE <arch_name> OF <ent_name> IS
    TYPE states IS (state0, state1, state2, state3, ...);
    SIGNAL pr_state, nx_state: states;
    SIGNAL temp: <data_type>;
BEGIN
    ----- Lower section: -----
    PROCESS (reset, clock)
    BEGIN
        IF (reset='1') THEN
            pr_state <= state0;
        ELSIF (clock'EVENT AND clock='1') THEN
            output <= temp;
            pr_state <= nx_state;
        END IF;
    END PROCESS;
```

VHDL> State Machines

Design Style #2 (Stored Output):

```
----- Upper section: -----  
PROCESS (pr_state)  
BEGIN  
    CASE pr_state IS  
        WHEN state0 =>  
            temp <= <value>;  
            IF (condition) THEN nx_state <= state1;  
            ...  
            END IF;  
        WHEN state1 =>  
            temp <= <value>;  
            IF (condition) THEN nx_state <= state2;  
            ...  
            END IF;  
        WHEN state2 =>  
            temp <= <value>;  
            IF (condition) THEN nx_state <= state3;  
            ...  
            END IF;  
        ...  
    END CASE;  
END PROCESS;  
END <arch_name>;
```