



جامعة نينوى  
كلية هندسة الإلكترونيات

# Circuit Design with VHDL 7

Textbook: Volnei A. Pedroni

Submitted By: Hussein Aideen

# VHDL> Sequential Code

---

- PROCESSES, FUNCTIONS, and PROCEDURES are executed sequentially.
- any of these blocks is still concurrent with any other statements placed outside it.
- with it we can build sequential circuits as well as combinational circuits.

# VHDL> Sequential Code

---

- IF, WAIT, CASE, and LOOP.
- VARIABLES restricted to be used in sequential code.

# VHDL> PROCESS

- A PROCESS must be installed in the main code.
- executed every time a signal in the sensitivity list changes.

```
[label:] PROCESS (sensitivity list)
    [VARIABLE name type [range] [:= initial_value;]]
BEGIN
    (sequential code)
END PROCESS [label];
```

# VHDL> PROCESS

---

- initial value is not synthesizable.
- monitoring a signal (clock, for example) is necessary. A common way of detecting a signal change is by means of the EVENT attribute.
- For instance, if clk is a signal to be monitored, then clk'EVENT returns TRUE when a change on clk occurs (rising or falling edge).

# VHDL> PROCESS

- IF statement:


```
IF conditions THEN assignments;  
ELSIF conditions THEN assignments;  
...  
ELSE assignments;  
END IF;
```

```
IF (x<y) THEN temp:="11111111";  
ELSIF (x=y AND w='0') THEN temp:="11110000";  
ELSE temp:=(OTHERS =>'0');  
end if
```
 
# VHDL> IF statement

- One-digit Counter #1
  - 1-digit decimal counter (0 → 9 → 0).


```
1  -----  
2  LIBRARY ieee;  
3  USE ieee.std_logic_1164.all;  
4  -----  
5  ENTITY counter IS  
6  PORT (clk : IN STD_LOGIC;  
7  digit : OUT INTEGER RANGE 0 TO 9);  
8  END counter;  
9  -----
```


 
# VHDL> IF statement

- One-digit Counter #1
  - 1-digit decimal counter ( $0 \rightarrow 9 \rightarrow 0$ ).


```
10 ARCHITECTURE counter OF counter IS
11 BEGIN
12   count: PROCESS (clk)
13   VARIABLE temp : INTEGER RANGE 0 TO 10;
14   BEGIN
15     IF (clk'EVENT AND clk='1') THEN
16       temp := temp + 1;
17       IF (temp=10) THEN temp := 0;
18     END IF;
19   END IF;
20   digit <= temp;
21 END PROCESS count;
22 END counter;
23 -----
```





# VHDL> IF statement

- 4 bit Shift Register:

 

```
1  -----  
2  LIBRARY ieee;  
3  USE ieee.std_logic_1164.all;  
4  -----  
5  ENTITY shiftreg IS  
6  GENERIC (n: INTEGER := 4); -- # of stages  
7  PORT (d, clk, rst: IN STD_LOGIC;  
8  q: OUT STD_LOGIC);  
9  END shiftreg;
```

# VHDL> IF statement

- 4 bit Shift Register:

```
--  
11  ARCHITECTURE behavior OF shiftreg IS  
12  SIGNAL internal: STD_LOGIC_VECTOR (n-1 DOWNT0 0);  
13  BEGIN  
14  PROCESS (clk, rst)  
15  BEGIN  
16  IF (rst='1') THEN  
17  internal <= (OTHERS => '0');  
18  ELSIF (clk'EVENT AND clk='1') THEN  
19  internal <= d & internal(internal'LEFT DOWNT0 1);  
20  END IF;  
21  END PROCESS;  
22  q <= internal(0);  
23  END behavior;  
24  -----
```

# VHDL> WAIT statement

- WAIT statement: (inside Process)
- the PROCESS cannot have a sensitivity list when WAIT is employed.

```
WAIT UNTIL signal_condition;
```

---

---

```
WAIT ON signal1 [, signal2, ... ];
```

---

---

```
WAIT FOR time;
```

Simulation only

# VHDL> WAIT statement

- WAIT statement:
- the PROCESS cannot have a sensitivity list when WAIT is employed.

Example: 8-bit\_register \_with synchronous reset.

```
PROCESS -- no sensitivity list
```

```
BEGIN
```

```
    WAIT UNTIL (clk'EVENT AND clk='1');
```

```
    IF (rst='1') THEN
```

```
        output <= "00000000";
```

```
    ELSIF (clk'EVENT AND clk='1') THEN
```

```
        output <= input;
```

```
    END IF;
```

```
END PROCESS;
```

# VHDL> WAIT statement

- WAIT ON:

Example: 8-bit\_register \_with asynchronous reset.

```
PROCESS
BEGIN
    WAIT ON clk, rst;
    IF (rst='1') THEN
        output <= "00000000";
    ELSIF (clk'EVENT AND clk='1') THEN
        output <= input;
    END IF;
END PROCESS;
```

- WAIT FOR is intended for simulation only (waveform generation for test-benches). Example: WAIT FOR 5ns;

# VHDL> WAIT statement

---

- Home Works:
- DFF with Asynchronous Reset #2, Page 99.
- One-digit Counter #2, Page 99-100.

# VHDL> CASE statement

- CASE statement:

```
CASE identifier IS  
    WHEN value => assignments;  
    WHEN value => assignments;  
    ...  
END CASE;
```

```
CASE control IS  
    WHEN "00" => x<=a; y<=b;  
    WHEN "01" => x<=b; y<=c;  
    WHEN OTHERS => x<="0000"; y<="ZZZZ";  
END CASE;
```

# VHDL> CASE statement



---

- CASE statement:
- CASE statement (sequential) is very similar to WHEN (combinational)
- keyword **OTHERS** is often helpful.
- Another important keyword is **NULL** (the counterpart of UNAFFECTED), which should be used when no action is to take place.
- CASE allows multiple assignments for each test condition.



# VHDL> CASE statement

- Two-digit Counter with SSD Output:

  

# VHDL> Two-digit Counter with SSD

```
1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY counter2digit IS
6  PORT (clk, reset : IN STD_LOGIC;
7  digit1, digit2 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0));
8  END counter2digit;
9  -----
10 ARCHITECTURE counter OF counter2digit IS
11 BEGIN
12 PROCESS (clk, reset)
13 VARIABLE temp1: INTEGER RANGE 0 TO 10;
14 VARIABLE temp2: INTEGER RANGE 0 TO 10;
15 BEGIN
16 ---- counter: -----
17 IF (reset='1') THEN
18 temp1 := 0;
19 temp2 := 0;
20 ELSIF (clk'EVENT AND clk='1') THEN
```

# VHDL> Two-digit Counter with SSD

```
20  ELSIF (clk'EVENT AND clk='1') THEN
21  temp1 := temp1 + 1;
22  IF (temp1=10) THEN
23  temp1 := 0;
24  temp2 := temp2 + 1;
25  IF (temp2=10) THEN
26  temp2 := 0;
27  END IF;
28  END IF;
29  END IF;
30  ---- BCD to SSD conversion: ----
```

# VHDL> Two-digit Counter with SSD

```
30  ---- BCD to SSD conversion: -----
31  CASE temp1 IS
32  WHEN 0 => digit1 <= "1111110"; --7E
33  WHEN 1 => digit1 <= "0110000"; --30
34  WHEN 2 => digit1 <= "1101101"; --6D
35  WHEN 3 => digit1 <= "1111001"; --79
36  WHEN 4 => digit1 <= "0110011"; --33
37  WHEN 5 => digit1 <= "1011011"; --5B
38  WHEN 6 => digit1 <= "1011111"; --5F
39  WHEN 7 => digit1 <= "1110000"; --70
40  WHEN 8 => digit1 <= "1111111"; --7F
41  WHEN 9 => digit1 <= "1111011"; --7B
42  WHEN OTHERS => NULL;
43  END CASE;
```


# VHDL> Two-digit Counter with SSD

```
44  CASE temp2 IS
45  WHEN 0 => digit2 <= "1111110"; --7E
46  WHEN 1 => digit2 <= "0110000"; --30
47  WHEN 2 => digit2 <= "1101101"; --6D
48  WHEN 3 => digit2 <= "1111001"; --79
49  WHEN 4 => digit2 <= "0110011"; --33
50  WHEN 5 => digit2 <= "1011011"; --5B
51  WHEN 6 => digit2 <= "1011111"; --5F
52  WHEN 7 => digit2 <= "1110000"; --70
53  WHEN 8 => digit2 <= "1111111"; --7F
54  WHEN 9 => digit2 <= "1111011"; --7B
55  WHEN OTHERS => NULL;
56  END CASE;
57  END PROCESS;
58  END counter;
59  -----
```
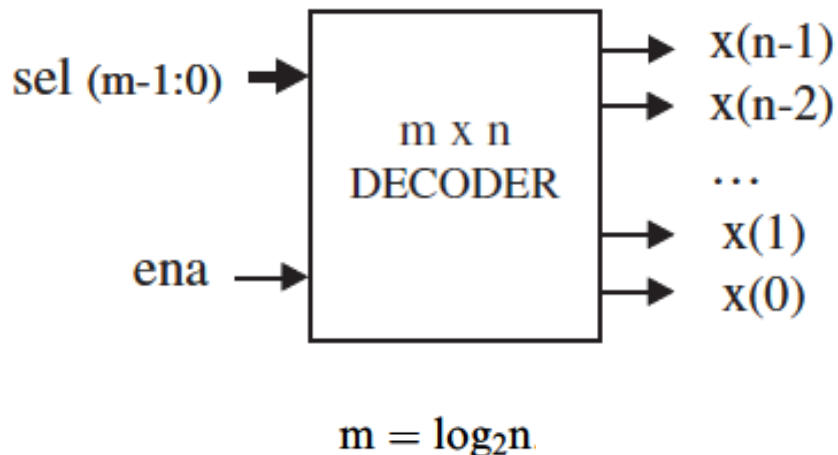
# VHDL> Examples

- Generic **Decoder:**

- If  $\text{ena} = '0'$ , then all bits of  $x$  should be high; otherwise, the output bit selected by  $\text{sel}$  should be low.



ena	sel	x
0	00	1111
1	00	1110
	01	1101
	10	1011
	11	0111

# VHDL> Examples

- **Generic Decoder:**

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY decoder IS
PORT ( ena : IN STD_LOGIC;
      sel : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
      x : OUT STD_LOGIC_VECTOR (7 DOWNTO 0));
END decoder;

ARCHITECTURE generic_decoder OF decoder IS
BEGIN
  PROCESS (ena, sel)
    VARIABLE temp1 : STD_LOGIC_VECTOR (x'HIGH DOWNTO 0);
    VARIABLE temp2 : INTEGER RANGE 0 TO x'HIGH;
  BEGIN
    temp1 := (OTHERS => '1');
    IF (ena='1') THEN
      temp2:=conv_integer(signed(sel));
      temp1(temp2):='0';
    END IF;
    x <= temp1;
  END PROCESS;
END generic_decoder;
```

# VHDL> Examples

- Gray code counter:

```
entity gray_counter is
  port (
    cout :out std_logic_vector (7 downto 0); -- Output of t
    enable :in std_logic;                    -- Enable counting
    clk :in std_logic;                       -- Input clock
    reset :in std_logic                      -- Input reset
  );
end entity;
```

```
architecture rtl of gray_counter is
  signal count :std_logic_vector (7 downto 0);
begin
  process (clk, reset) begin
    if (reset = '1') then
      count <= (others=>'0');
    elsif (rising_edge(clk)) then
      if (enable = '1') then
        count <= count + 1;
      end if;
    end if;
  end process;
```

```
    cout <= (count(7) &
      (count(7) xor count(6)) &
      (count(6) xor count(5)) &
      (count(5) xor count(4)) &
      (count(4) xor count(3)) &
      (count(3) xor count(2)) &
      (count(2) xor count(1)) &
      (count(1) xor count(0)) );
end architecture;
```

binary	gray
000	000
001	001
010	011
011	010
100	110
101	111
110	101
111	100