



جامعة نينوى  
كلية هندسة الإلكترونيات

# Circuit Design with VHDL 8

Textbook: Volnei A. Pedroni

Submitted By: Hussein Aideen

# VHDL> Loop statement

- LOOP is useful when a piece of code must be instantiated several times.
- inside a PROCESS, FUNCTION, or PROCEDURE.
- FOR / LOOP: repeated a fixed number of times.

```
[label:] FOR identifier IN range LOOP  
    (sequential statements)  
END LOOP [label];
```

```
FOR i IN 0 TO 5 LOOP  
    x(i) <= enable AND w(i+2);  
    y(0, i) <= w(i);  
END LOOP;
```

# VHDL> Loop statement

- WHILE / LOOP: repeated until a condition no longer holds.

```
[label:] WHILE condition LOOP  
    (sequential statements)  
END LOOP [label];
```

```
WHILE (i < 10) LOOP  
    WAIT UNTIL clk'EVENT AND clk='1';  
    (other statements)  
END LOOP;
```

# VHDL> Loop statement

- EXIT: Used for ending the loop.

```
[label:] EXIT [label] [WHEN condition];
```

- NEXT: Used for skipping loop steps.


```
[label:] NEXT [loop_label] [WHEN condition];
```

# VHDL> Loop statement

- Simple Barrel Shifter:
- The circuit must shift the input vector (of size 8) either 0 or 1 position to the left. When actually shifted (shift = 1), the LSB bit must be filled with '0' (shown in the bottom left corner of the diagram).
- If shift = 0, then  $\text{outp} = \text{inp}$ ;
- if shift = 1, then  $\text{outp}(0) = '0'$  and  $\text{outp}(i) = \text{inp}(i - 1)$ , for  $1 \leq i \leq 7$ .
 
# VHDL> Loop statement

- If  $\text{shift} = 0$ , then  $\text{outp} = \text{inp}$ ;
- if  $\text{shift} = 1$ , then  $\text{outp}(0) = '0'$  and  $\text{outp}(i) = \text{inp}(i - 1)$ , for  $1 \leq i \leq 7$ .




# VHDL> Simple Barrel Shifter

```
1  -----  
2  LIBRARY ieee;  
3  USE ieee.std_logic_1164.all;  
4  -----  
5  ENTITY barrel IS  
6  GENERIC (n: INTEGER := 8);  
7  PORT ( inp: IN STD_LOGIC_VECTOR (n-1 DOWNT0 0);  
8        shift: IN INTEGER RANGE 0 TO 1;  
9        outp: OUT STD_LOGIC_VECTOR (n-1 DOWNT0 0));  
10 END barrel;  
11 -----
```
 
# VHDL> Simple Barrel Shifter

```
11 -----
12 ARCHITECTURE RTL OF barrel IS
13 BEGIN
14     PROCESS (inp, shift)
15     BEGIN
16         IF (shift=0) THEN
17             outp <= inp;
18         ELSE
19             outp(0) <= '0';
20             FOR i IN 1 TO inp'HIGH LOOP
21                 outp(i) <= inp(i-1);
22             END LOOP;
23         END IF;
24     END PROCESS;
25 END RTL;
26 -----
```





 
# VHDL> Examples

- Generic Parity **Generator**:


- The circuit must add one bit to the input vector (on its left).
- Such bit must be a '0' if the number of '1's in the input vector is even, or a '1' if it is odd, such that the resulting vector will always contain an even number of '1's (even parity).


 
# VHDL> Examples


- Generic Parity Generator:

```
-----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
-----  
ENTITY parity_gen IS  
  GENERIC (n : INTEGER := 7);  
  PORT ( input: IN STD_LOGIC_VECTOR (n-1 DOWNTO 0);  
        output: OUT STD_LOGIC_VECTOR (n DOWNTO 0));  
END parity_gen;  
-----  
ARCHITECTURE parity OF parity_gen IS  
BEGIN  
  PROCESS (input)  
    VARIABLE temp1: STD_LOGIC;  
    VARIABLE temp2: STD_LOGIC_VECTOR (output'RANGE);  
  BEGIN  
    temp1 := '0';  
    FOR i IN input'_RANGE LOOP  
      temp1 := temp1 XOR input(i);  
      temp2(i) := input(i);  
    END LOOP;  
    temp2(output'HIGH) := temp1;  
    output <= temp2;  
  END PROCESS;  
END parity;
```


 
# VHDL> Examples

- Generic Parity Detector:
- The circuit must provide output = '0' when the number of '1's in the input vector is odd, or output = '1' otherwise.



# VHDL> Examples

- Generic Parity Detector:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY parity_det IS
GENERIC (n : INTEGER := 7);
PORT ( input: IN Std_logic_VECTOR (n DOWNTO 0);
output: out Std_logic);
END parity_det;

-----

ARCHITECTURE parity OF parity_det IS
BEGIN
PROCESS (input)
VARIABLE temp: Std_logic;
BEGIN
temp := '0';
FOR i IN input'RANGE LOOP
temp := temp XOR input(i);
END LOOP;
output <= not temp;
END PROCESS;
END parity;
```

